

<div style="text-align: justify;">Stm❖a? pracuje tak, ❖e pokud na b❖i fototranzistoru T1 dopad❖sv?tlo, tranzistor T2 nen❖sepnut a tedy nesv❖❖ani LED1 nebo nen❖sepnut v❖stup OUT. Jakmile se fototranzistor zast❖❖ T1 sepne. Citlivost lze nastavit trimrem R1.
</div> <div style="text-align: justify;">.
</div> <div style="text-align: justify;">.
</div> <div>Sch❖a:
</div> <div></div> <div>.
</div> <div>Plo❖n❖ spoj:
</div> <div></div> .
 <div>PDF verze: sch❖a, plo❖n❖ spoj 1:1 (40x20mm), osazovac❖pl❖</div> <div>Eagle 5.11: SCH a BRD + doporu?en❖P❖ovo knihovna sou?❖tek #PaJa_22.lbr. </div> <div>
</div> <div>Deska byla vyrobena metodou na❖ehlen❖ tonneru.
</div> <div>
</div> <div>Seznam pou❖it❖ch sou?❖tek:</div> <div>
</div> <div>R1 - Trimr 1M
</div> <div>R2 - 1k - velikost 0207</div> <div>R3 - 10k - velikost 0207</div> <div>R4 - 100R - velikost 0207</div> <div>
</div> <div>T1 - LL505 - 2mm - Odkaz
</div> <div>T2 - BC547 nebo jin❖ NPN tranzistor
</div> <div>
</div> <div>LED1 - sv❖ic❖dioda, 5mm</div> <p></p> <p>
video:</p> <hr /> <div>.</div> <div>.</div> <div>.</div> <div>.</div> <div style="text-align: center;"><a target="_blank"

Jednoduchá stmá?

Napsal uživatel Kroužek elektroniky
Čtvrtek, 22. prosinec 2011 21:09

```
#ffffff;".</span></div> <div><span style="color: #ffffff;".</span></div> <div><span  
style="color: #ffffff;".</span></div> <div><span style="color: #ffffff;".</span><br /> <hr />  
</div>
```